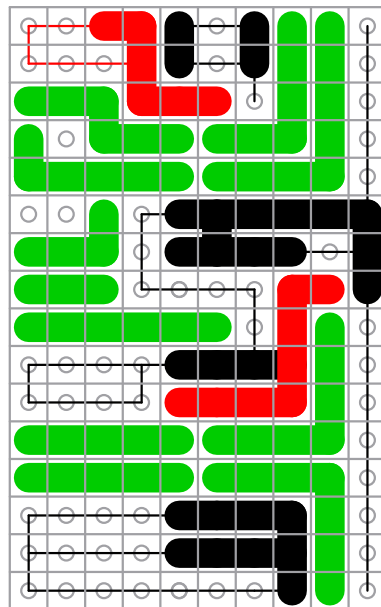
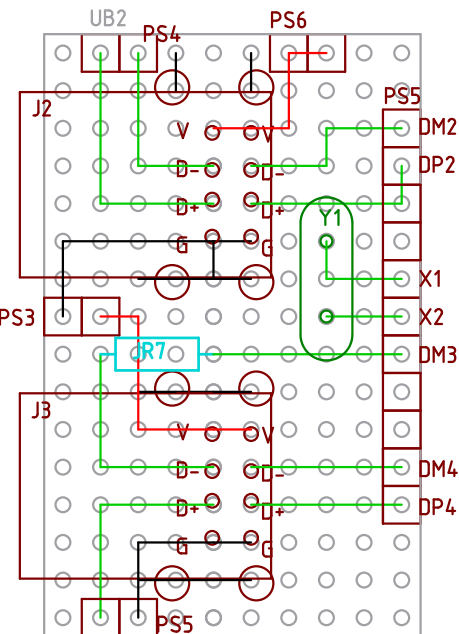
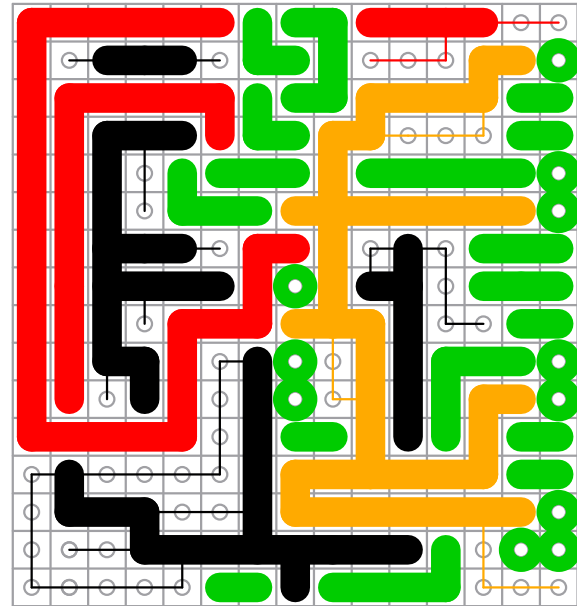
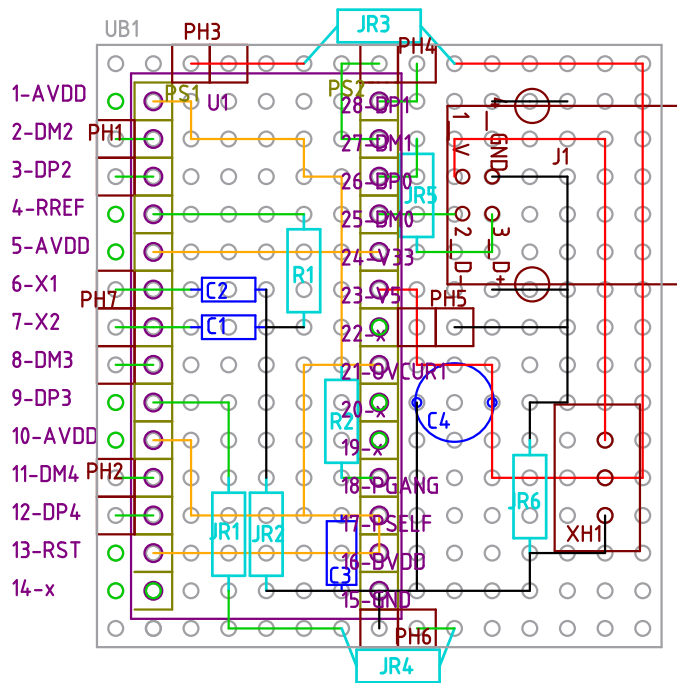


C1,2: 15pF  
 C3: 1uF  
 C4: 220uF  
 J1: USB B jack  
 JR1-6: Jumper wire  
 PH1-6: pin header 2P  
 PH7: pin header 3P  
 PS1-2: pin socket 14P  
 R1: 680 ohm  
 R2: 100k ohm  
 UB1: universal board 15x16  
 XH1: XHP header 3P



J2,3: USB A2 Jack  
 JR7: jump wire  
 PS3-6: pin socket 2P H=3.5  
 PS7: pin socket 11P H=3.5  
 UB2: 10x16P  
 Y1: crystal 12MHz